

FACULTY OF SCIENCE
SCHOOL OF BASIC SCIENCES
BCA – I Semester
Make-up Examination: 2018-19
CA 1102 – Fundamentals of Digital Electronics
(CLOSED BOOK)

Duration: 3 Hours

Max. Marks: –100

Instructions:

- Answer any five full questions
- Missing data, if any, may be assumed suitably.

1. a) Show That : [4]
(i) $B+B'C=B+C$

(ii) $(X+Y)(X+Z)=X+YZ$

- b) (i) $(1BC)_{16} = (?)_8$ (ii) $(12.48)_{10} = (?)_2$ [8]

(iii) $(110.111)_2 = (?)_{10}$ (iv) $(534)_8 = (?)_{16}$

- c) Perform Binary Arithmetics: [8]

(i) $(34)_{10} + (39)_{10}$ (ii) $(38)_{10} - (23)_{10}$

(iii) $(11101)_2 * (110)_2$ (iv) $(100100)_2 / (100)_2$

2. a) Distinguish between sum-of-Products and Product-of-sum form. [4]

- b) Use Boolean algebra techniques, simplify following expressions: [6]

(i) $AB+A(B+C)+B(B+C)$

(ii) $[AB'(C+BD)+A'B']C$

- c) In a 7-segment display, each of the seven segments is activated for various digits. For example, segment *a* is activated for the digits 0,2,3,5,6,7,8 and 9 as shown in the figure. find the expression for each segment using the variables A,B,C,D and minimize the expression using K-Map. [10]



3. a) Discuss Don't care conditions in brief. [4]

- b) What are universal gates? Construct a logic circuit using NAND gates only for the Expression $x = A \cdot (B + C)$. [6]

- c) Develop look-ahead carry logic for adders. State the advantage of look ahead carries addition. Define *carry generation* (C_g) and *carry propagation* (C_p) and explain the difference between C_g and C_p . [10]

4. a) Design a 4-bit Gray-to-Binary converter using truth table, K-maps, and logic Diagram. [10]
- b) Determine and draw the logic required to decode the binary number 1011 by producing a **HIGH** level on the input. [10]
5. a) Give the difference between synchronous and asynchronous sequential circuit. [4]
- b) What is a **S-R** latch? Develop an excitation table for active-HIGH input **S-R** latch. [6]
- c) What do you mean by toggle? Explain the function of a J-K flip flop using a Suitable diagram and discuss how it works. [10]
6. a) Explain the operation of 16:1 multiplexer with the help of logic circuit. [10]
- b) Define race around condition? Explain in detail the operation of master-slave flip-flop and show how the race around condition is eliminated in it. [10]